

INDEX

Electrical Basics Drawing Samples

Basics 1	Overall Plant 1-Line
Basics 2	7.2 kV Bus 1-Line
Basics 3	4.16 kV Bus 1-Line
Basics 4	600 V 1-Line
Basics 5	480 V MCC 1-Line
Basics 6	7.2 kV 3-Line Diagram
Basics 7	4.16 kV 3-Line Diagram
Basics 8	AOV Elementary & Block Diagram
Basics 9	4.16 kV Pump Schematic
Basics 10	480 V Pump Schematic
Basics 11	MOV Schematic (with Block included)
Basics 12	12-/208 VAC Panel Diagram
Basics 13	Valve Limit Switch Legend
Basics 14	AOV Schematic (with Block included)
Basics 15	Wiring (or Connection) Diagram
Basics 16	Wiring (or Connection) Diagram
Basics 17	Tray & Conduit Layout Drawing
Basics 18	Embedded Conduit Drawing
Basics 19	Instrument Loop Diagram

INDEX

Handout References

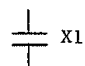
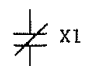
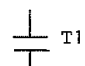
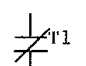
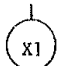
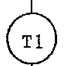
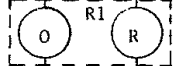
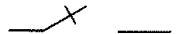

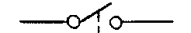
Reference 1	Index for Handouts & Basic Drawings
Reference 2	Electrical Drawing Symbols
Reference 3	IEEE Device Numbers
Reference 4	Circuit Analysis Worksheet Template
Reference 5	Example Problems Electrical 1-Line Diagram
Reference 6	Schematic & Device Legend
Reference 7	SOV Schematic Diagram Example
Reference 8	MOV Schematic Diagram Example
Reference 9	Breaker Schematic Diagram Example
Reference 10	Task 3 / 9A Recommended Process Cheat Sheet
Reference 11	List of Circuit Analysis Exercises

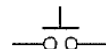
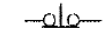
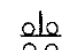
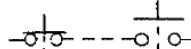
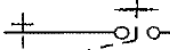
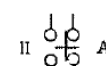
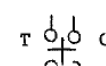


TYPICAL ELECTRICAL DRAWING SYMBOLS AND CONVENTIONS







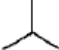

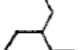
ELECTRICAL SYMBOLS





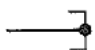

◆ Denotes common symbols we will encounter in the sample problems


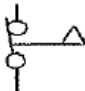

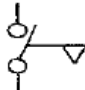

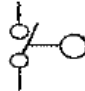
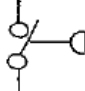
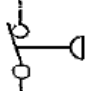
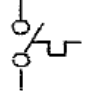
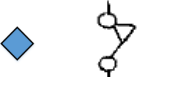

CONTACTS, SWITCHES, CONTACTORS AND RELAYS

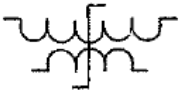


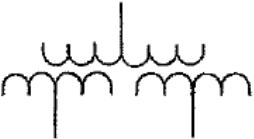
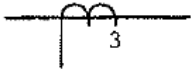
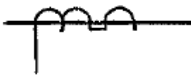
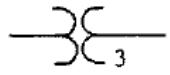
SYMBOL	DESCRIPTION
◆  X1  X1 N.O. N.C.	Relay contact - Shown with relay in de-energized or in reset position. (Show relay coil designation near contact.)
◆  T1  T1 TDC TDO	Timing Relay Contact - TDC indicates contact closes at end of timing period. TDO contact opens at end of timing period.
◆  X1	Coil - Relay, contactors, circuit breaker, solenoid etc. (Show device designation, X1)
◆  T1 TDC	Coil - Timing Relay - TDC indicates timing period starts when coil is energized. TDO indicates timing period starts when coil is de-energized.
	Latching Relay or Mechanically-Held Contactor O=operate; R=reset; TC=trip coil; CC=closing coil. (Coils may be separated on diagram)
	Knife Switch, general. (If shown closed, terminals must be added.)
◆ 	Switch - General, single pole, single throw.
◆ 	Switch - One pole of multi-pole switch shown. Other poles shown elsewhere.



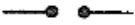



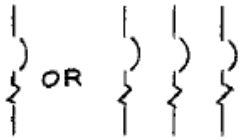

◆ 	Pushbutton - Momentary or spring return. Single Circuit (make)
◆ 	Pushbutton - Momentary or spring return. Single Circuit (break)
	Pushbutton - Momentary or spring return. Two Circuit
	Pushbutton - Maintained, two circuit
	Pushbutton - Maintained, single circuit
	Selector Switch - Two position, maintained - (designate position shown; i.e. A=Auto; B=Hand)
	Selector Switch - Three position, SR indicates spring return from position so labeled. ("TRIP-(NORMAL)-CLOSE" position shown)
◆ 	Limit Switch - Normally open - Not applicable for Motor Operated Valves and Solenoid Valves.
◆ 	Limit Switch - Normally closed - Not applicable for Motor Operated Valves and Solenoid Valves.

	Used with other symbols to indicate device is adjustable
 (Positive)  (Negative)	Polarity markings - Direct current.
	Instantaneous Polarity Markings
	3-phase, 3-wire, delta
	3-phase, 3-wire, open delta grounded
	3-phase, 3-wire, wye
	3-phase, 3-wire, wye grounded neutral
	3-phase, 3-wire, zigzag

	3-phase, 3 wire zigzag, grounded neutral
	Connection to earth ground (may be plant grounding system)
	Connection to chassis or frame
	Terminal - may be added to any of the following symbols at connection points.
	Short circuit (not a fault)
	Terminal - Designates termination point of field run cables to main control board, emergency power board, main control board termination cabinet or emergency power board termination cabinet.

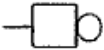
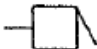
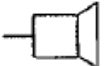
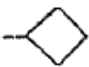

	Flow Switch - Closes on increase in flow at value shown
	Flow Switch - Opens on increase in flow at value shown
	Flow Switch - Closes on decrease in flow at value shown.
	Flow Switch - Opens on decrease in flow at value shown.
	Liquid Level - Opens on rising level Switch (Closes on low level)
	Liquid Level - Closes on rising level Switch (Opens on low level)
	Pressure or Vacuum - Closes on rising pressure Switch
	Pressure or Vacuum - Opens on rising pressure Switch (Closes on increase in vacuum)
	Temperature Switch - Closes on increasing temp.
	 Torque Switch - Opens on high torque (Motor Operated Valves)

		Transducer - Control winding shown with 5 loops. Power winding shown with 3 loops.
◆		Transformer - General, two winding
		Autotransformer - General
		Transformer - General, three winding
◆		Current Transformer - number represents quantity (Add instantaneous polarity marks and ratio)
		Bushing Type Current Transformer
◆		Potential Transformer - number represents quantity (Show instantaneous polarity marks, voltage rating, vectors, etc.)

◆		Fuse - General
		High Voltage Primary Fuse Cutout
		Lightning Arrester - General Gap Type
		Lightning Arrester - Valve or film type
◆		Circuit Breaker - General
◆		Power Circuit Breaker - (Show location of operating mechanism)
◆		Circuit Breaker, 3-pole with magnetic - overload device in each pole. (Show rating)
◆		Circuit Breaker, 3-pole, drawout type (Used in metal clad switchgear groups)

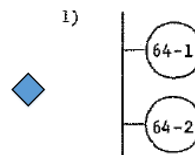
2

INDICATORS & ALARMS

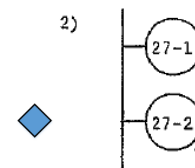
	Bell, electric
	Buzzer
	Horn - General
	Annunciator - General
	Indicating Light - General
<p>Use the following to specify color:</p> <p>A - Amber B - Blue C - Clear G - Green NE - Neon O - Orange OP - Opalescent P - Purple R - Red W - White Y - Yellow</p>	

RELAYS

The following methods are used on drawings to identify relays:

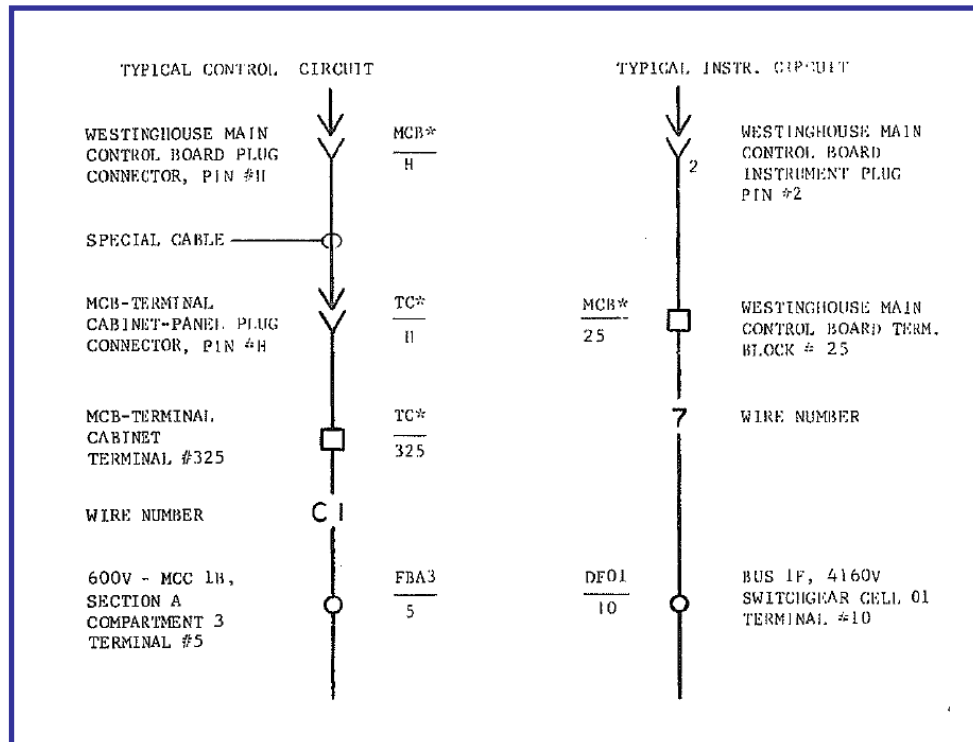


Two (2) 64 devices 64-1 and 64-2 in same cell.



Three (3) 27 devices 27-1, 27-2 and 27-3. The two (2) below the 27-2 device indicates there are two (2) 27 devices and their sequence numbers are in numerical order starting with -2.

ELEMENTARY DIAGRAM CONNECTIONS



*Abbreviation for equipment - The corresponding equipment number will appear in a table on the elementary diagram (e.g. MCB = Q1112C005)

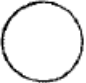








WIRE NUMBERING



WIRE NUMBERING SYSTEM

1. The following standard interconnecting wire numbers shall be used wherever applicable (for computer - schedule programming).

Wire Number	Purpose	Wire Number	Purpose
1	A - Phase Power	4	A - Phase Potential
2	B - Phase Power		(See Notes 3 & 5)
3	C - Phase Power	5	A - Phase Current
(Note 1)	Annunciator		(See Notes 3 & 5)
N	D. C. Negative (See Note 2)	6	B - Phase Potential
P	D. C. Positive (See Note 2)		(See Notes 3 & 5)
U	115 volt A. C.-Ground Return (see Note 2)	7	B Phase Current
X	115 volt A. C. (See Note 2)		(see Notes 3 & 5)
C	Closing (See Note 2)	8	C - Phase Potential
T	Tripping (See Note. 2).		(See Notes 3 & 5)
O	Opening, MOV Only (See Note 2)	9	C - Phase Current
F	Instrumentation (e.g. indicator, recorder, etc) (See Note 2)		(See Notes 3 & 5)
H	Computer (See Note 2)		
M	General Control (Neither tripping nor closing; See Note 2)	0	Potential (or Current) Neutral (See Notes 4 & 5)
A	Amber Lamp (See Note 2)		
B	Blue Lamp (See Note 2)		
L	Green Lamp (See Note 2)		
R	Red Lamp (See Note 2)		
W	White Lamp (See Note 2)		

Understanding these general conventions will greatly help with understanding of how to work with schematic (elementary) diagrams

	Basic, Generator or Motor
	Field, Compensating, Generator or Motor
	Field, Series, Generator or Motor
	Field, Short or Separately Excited, Generator or Motor
	Field, Permanent Magnet, Generator or Motor
	1-phase
	2-phase
	3-phase, wye 

	3-phase wye, grounded
	3-phase delta

ABBREVIATIONS

◆	A	Ammeter	◆	PI	Position indicator
	Ah	Ampere-hour		RD	Recording demand meter
	C	Coulombmeter		REC	Recording
	CMA	Contact-making (or breaking) ammeter		RF	Reactive factor
	CMC	Contact-making (or breaking) clock		SY	Synchroscope
	CMV	Contact-making (or breaking) voltmeter		t ^o	Temperature meter
	CRO	Oscilloscope or cathoderay oscillograph		THC	Thermal converter
	DB	DB (decibel) meter Audio level/meter		TLM	Telemeter
	DBM	DBM (decibels referred to 1 milliwatt (meter))		TT	Total time; Elapsed time
	DM	Demand meter	◆	V	Voltmeter
	DTR	Demand-totalizing relay		VA	Volt-ammeter
◆	F	Frequency meter		VAR	Varmeter
	G	Galvanometer		VARH	Varhour meter
	GD	Ground detector		VI	Volume indicator; Meter, audio level
	I	Indicating		VU	Standard volume indicator Meter, audio level
	INT	Integrating	◆	W	Wattmeter
	UA	Microammeter		WH	Watthour meter
	MA	Milliammeter			
	NM	Noise meter			
	OHM	Ohmmeter			
	OP	Oil pressure			
	OSCG	Oscillograph, string			
	PF	Power factor			
	PII	Phasemeter			

ANSI/IEEE Standard Device Numbers

1 – Master Element	39 – Mechanical Condition Monitor
2 – Time delay Starting or Closing Relay	40 – Field (over/under excitation) Relay
3 – Checking or Interlocking Relay	41 – Field Circuit Breaker
4 – Master Contactor	42 – Running Circuit Breaker
5 – Stopping	43 – Manual Transfer or Selector Device
6 – Starting Circuit Breaker	44 – Unit Sequence Starting Relay
7 – Rate of Change Relay	45 – DC over voltage Relay
8 – Control Power Disconnecting Device	46 – Reverse-phase or Phase-Balance Current Relay
9 – Reversing Device	47 – Phase-Sequence or Phase-Balance Voltage Relay
10 – Unit Sequence Switch	48 – Incomplete Sequence Relay
11 – Multi-function Device	49 – Machine or Transformer, Thermal Relay - OLR
12 – Overspeed Device	50 – Instantaneous Overcurrent Relay
13 – Synchronous-speed Device	50G - Instantaneous Earth Overcurrent Relay (Neutral CT Method)
14 – Underspeed Device	50N - Instantaneous Earth Overcurrent Relay (Residual Method)
15 – Speed – or Frequency, Matching Device	50BF - Breaker failure
16 – Data Communications Device	51 – AC Inverse Time Overcurrent Relay
17 – Shunting or Discharge Switch	51G - AC Inverse Time Earth Overcurrent Relay (Neutral CT Method)
18 – Accelerating or Decelerating Device	51N - AC Inverse Time Earth Overcurrent Relay (Residual Method)
19 – Starting to Running Transition Contractor	52 – AC Circuit Breaker
20 – Electrically Operated Valve	52a - AC Circuit Breaker Position (Contact Open when Breaker Open)
21 – Distance Relay	52b - AC Circuit Breaker Position (Contact Closed when Breaker Open)
22 – Equalizer Circuit Breaker	53 – Exciter or DC Generator Relay
23 – Temperature Control Device	54 – Turning Gear Engaging Device
24 – Volts per Hertz Relay	55 – Power Factor Relay
25 – Synchronizing or Synchronize-Check Device	56 – Field Application Relay
26 – Apparatus Thermal Device	57 – Short-Circuiting or Grounding Device
27 – Undervoltage Relay	58 – Rectification Failure Relay
27s - DC under voltage Relay	59 – Overvoltage Relay
28 – Flame detector	60 – Voltage or Current Balance Relay.
29 – Isolating Contactor or Switch	61 – Density Switch or Sensor
30 – Annunciator Relay	62 – Time-Delay Stopping or Opening Relay
31 – Separate Excitation	63 – Pressure Switch
32 – Directional Power Relay or Reverse Power Relay	64 – Ground Detector Relay
33 – Position Switch	64R - Restricted earth fault
34 – Master Sequence Device	64S - Stator earth fault
35 – Brush-Operating or Slip-Ring Short-Circuiting Dev	65 – Governor
36 – Polarity or Polarizing Voltage Devices	66 – Notching or Jogging Device
37 – Undercurrent or Underpower Relay	67 – AC Directional Overcurrent Relay
38 – Bearing Protective Device	68 – Blocking Relay

ANSI/IEEE Standard Device Numbers

69 – Permissive Control Device

70 – Rheostat

71 – Liquid Level Switch

72 – DC Circuit Breaker

73 – Load-Resistor Contactor

74 – Alarm Relay

75 – Position Changing Mechanism

76 – DC Overcurrent Relay

77 – Telemetry Device

78 – Phase-Angle Measure Relay or "Out-of-Step" Relay

79 – AC Reclosing Relay (Auto Reclosing)

80 – Flow Switch

81 – Frequency Relay

82 – DC Reclosing Relay

83 – Automatic Selective Control or Transfer Relay

84 – Operating Mechanism

85 – Communications, Carrier, or Pilot-Wire Relay

86 – Lockout Relay/Master Trip

87 – Differential Protective Relay

88 – Auxiliary Motor or Motor Generator

89 – Line Switch

90 – Regulating Device

91 – Voltage Directional Relay

92 – Voltage and Power Directional Relay

93 – Field Changing Contactor

94 – Tripping or Trip-Free Relay (trip circuit supervision Relay)

95 – For specific applications where other numbers are not suitable

96 – Busbar Trip Lockout relay

97 – Specific applications where other numbers are not suitable

98 – Specific applications where other numbers are not suitable

99 – Specific applications where other numbers are not suitable

150 – Earth Fault Indicator

AFD – Arc Flash Detector

CLK – Clock or Timing Source

DDR – Dynamic Disturbance Recorder

DFR – Digital Fault Recorder

DME – Disturbance Monitor Equipment

HIZ – High Impedance Fault Detector

HMI – Human Machine Interface

HST – Historian

LGC – Scheme Logic

MET – Substation Metering

PDC – Phasor Data Concentrator

PMU – Phasor Measurement Unit

PQM – Power Quality Monitor

RIO – Remote Input/Output Device

RTU – Remote Terminal Unit/Data Concentrator

SER – Sequence of Events Recorder

TCM – Trip Circuit Monitor

LRSS - LOCAL/REMOTE SELECTOR SWITCH

SOTF - Switch On To Fault

DEVICE SUFFIX NUMBERS

A suffix letter or number may be used with the device number; for example, suffix N is used if the device is connected to a Neutral wire (example: 59N in a relay is used for protection against Neutral Displacement); and suffixes X,Y,Z are used for auxiliary devices.

Similarly, the "G" suffix can denote a "ground", hence a "51G" is a time overcurrent ground relay. The "G" suffix can also mean "generator", hence an "87G" is a Generator Differential Protective Relay while an "87T" is a Transformer Differential Protective Relay. "F" can denote "field" on a generator or "fuse", as in the protective fuse for a pickup transformer. Suffix numbers are used to distinguish multiple "same" devices in the same equipment such as 51-1, 51-2.

Common suffixes:	B – Bus	G – Ground or Generator
	F – Field	N - Neutral
	T – Transformer	

Device numbers may be combined if the device provides multiple functions, such as the instantaneous/time-delay AC over current relay denoted as 50/51.

[illegible]

Indication



D-207001- SINGLE LINE ELEC AUX
SYSTEM (EMERG- 4160v { 6000v})

D-207005- SINGLE LINE PROTECTION
§ METERING 4160V SWITCH
GEAR BUS 2F

D-207006- SINGLE LINE PROTECTION
§ METERING 4160V SWITCH
GEAR BUS 2S

A-117538- ELEC GENERAL DETAILS
§ NOTES

B-205810- LOGIC DIAG- SHEET 22

Cable Selection /Circuit Analysis

Recommended Process for Task 3 & Task 9A

Preparation

1. Collect Drawings
2. Understand functional state requirements of the circuit
3. Decide on:

Active functional state - Power is required to meet function state requirements

or

Passive functional state – Power is not required to meet function state requirements

Power Supply

4. Identify power supply and breaker/fuse for the circuit
5. Is power required to achieve/maintain functional state?
6. Determine requirement for “Alternate” power (if applicable)

Contact Positions / Cable-Conductor Markup

7. Mark up contact positions on drawings for “**Initial**” condition or state (*Don’t guess, use limit switch legends and switch developments*)
8. Highlight schematic (elementary) & block diagrams to show cable - conductor relationship

Hot-Probe Assessment

9. Using Hot-Probe and Ground-Probe technique, identify failure mode(s) for each conductor

NOTE: Remember that this technique for Task 3/9A assumes a “source” conductor is present and does not distinguish between intra-cable and inter-cable hot short
10. Assign Fault Codes to the conductors
11. Roll up conductor failure modes to cable(s)

Off-Scheme Circuits / Dependencies

12. Assess each control contact from off-scheme circuits (auxiliary contacts) to decide if it can impact the function state:
 - Is contact needed for proper operation of a credited automatic function

Cable Selection /Circuit Analysis

Recommended Process for Task 3 & Task 9A

- Could contact prevent automatic or manual operation
 - Could contact by itself (or in conjunction with another circuit failure) cause a spurious operation
13. If contact could affect function state, then an “Equipment Dependency” exists with the contact’s circuit.

Document Analysis

14. Document analysis per established process
15. File all markup drawings and notes in component work package (Current “Best Practice” is create electronic work package)
16. Generate failure reports as required to support PRA quantification

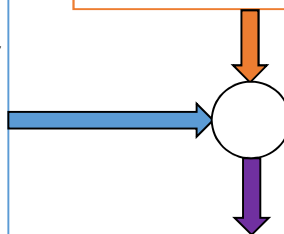
Fault Codes

Primary Circuit Failure Mode Descriptions

EI	Erroneous Indication
EIS	Erroneous Indicating Signal
LIS	Loss of Indicating Signal
LOC	Loss of Control
LOCP	Loss of Control Power (usually applies only to metalclad switchgear that depend on a separate control power source to actuate)
LOI	Loss of Indication
LOP	Loss of Power (to the circuit)
SA	Spuriously Actuates or Spuriously Actuation
SC	Spuriously Closes
SO	Spuriously Opens
SS	Spuriously Starts/Runs

Causal Modifiers

BF	Blown Fuse
HS	Hot Short
PR	Protective Relay
SG	Short to Ground



Example Usage:

LOP-BF:	Loss of power due to a blown fuse
SO-HS:	Spuriously opens due to a hot short
LOC-PR:	Loss of control due to a protective relay

List of Circuit Analysis Exercises (2019 Course)

Example No.	Component	Description of Example	Function State
1A	AOV-8879B	Easy AOV circuit with function states involving change of position and maintain energized position [Walkthrough Example]	Open - Closed
1B			Open - Open
2A	MOV-8112-A	Medium MOV circuit with interlock dependencies; various function states investigated [Walkthrough Example]	Closed - Open
2B			Closed - Closed
2C			Open - Closed
3A	MOV-8888	Easy MOV circuit with function states involving change of position and maintain initial position	Open - Open
3B			Open - Closed
4A	AOV-2869A	Medium difficulty AOV circuit with function states involving change of position and maintain position	Closed - Closed
4B			Closed - Open
5	MOV-11	DC MOV control circuit with desired change of state	Close - Open
6A	MOV-15	Double pole DC motor control circuit with desired change of state – remote and local operation	Close - Throttled
6B			Close – Throttled (Local)
7A	CCW Pump 1B	Medium difficulty 4.16 kV pump involving change of position and maintain position	Standby – On
7B			Off - Off
8	MCC-1B	480V MCC	Energized - Energized
9	LC-B	480V Load Center	Energized – Energized (Norm)
10	ANN-1	Annunciator Circuit	Available – Nonspurious
11	FCV-605A	Instrument control signal to flow control valve	Closed - Modulate
12	TTR2	Instrument loop – temperature indicator	Available – Available (FT-605A)
13	COMP-1	480 V Motor	Cycle - Cycle